


1. **Motivation:** The inspiration for developing a multifunctional signal generator stems from the critical need for versatile and precise signal sources in various scientific and engineering applications. Whether in educational settings, research labs, or industrial environments, having a single device that can produce sine, square, triangle, and pulse waveforms with adjustable amplitude and frequency significantly enhances experimentation and prototyping efficiency. This project aims to bridge the gap between affordability and functionality, providing an accessible yet powerful tool to support a wide range of electronic and signal processing projects.
2. **Problem Statement:** To develop a multifunctional signal generator capable of producing various waveform outputs, including sine, square, triangle, and pulse waves. This versatile device allows users to customize both the amplitude and frequency of the generated signals, making it suitable for a wide range of applications such as testing and troubleshooting electronic circuits, designing and analyzing audio equipment, and educational purposes in laboratories.

The signal generator will incorporate user-friendly controls for adjusting the amplitude and frequency within predefined ranges. These ranges will be selected to cover typical values required in most practical scenarios, ensuring the device's applicability in different fields. The amplitude adjustment will enable users to set the desired voltage level of the output signal, while the frequency adjustment will allow the selection of the signal's oscillation rate.

**Specifications:**

- Types of Waveforms: Sine, square, triangle, and pulse
- Power supply: 13V
- Minimum Frequency: 10 Hz
- Maximum Frequency: 100Hz
- Minimum Amplitude: 2V peak-to-peak
- Maximum Amplitude: 16V peak-to-peak (adjustable with amplitude control)
- Adjustable Duty Cycle:
- 6 Pin Push Switch: Accepting 12V and 13V DC

### 3. Design Procedure:

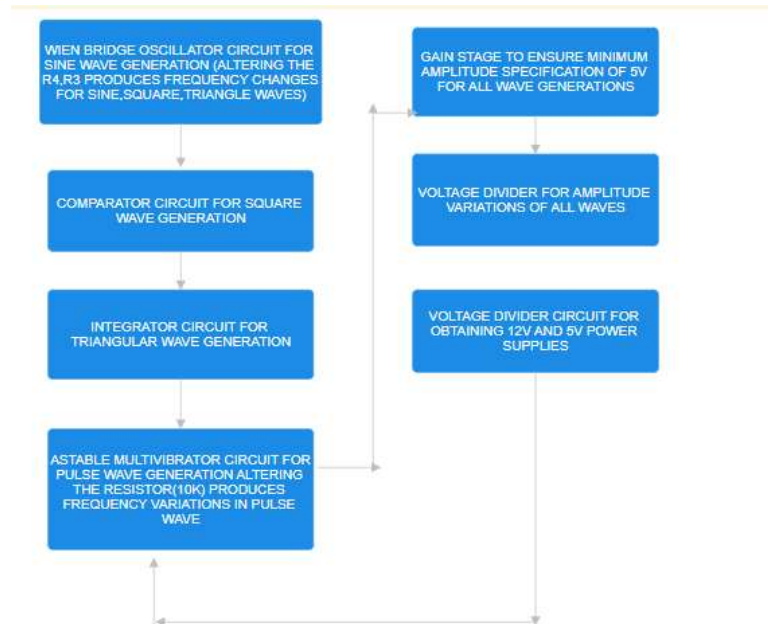


### 4. Budget:


COMPONENT	QUANTITY	COST
IC555 Timer	1	₹ 5
Op-amp ua741	6	₹ 60
6 Pin Push Switch	5	₹ 25
Potentiometer-10k	1	₹ 10
Potentiometer-47k	3	₹ 30
Breadboard	1	₹ 100
	<b>Total</b>	<b>₹ 230</b>

### 5. Circuit Diagram / Board Layout / Schematic:


#### (i) Sine Wave:

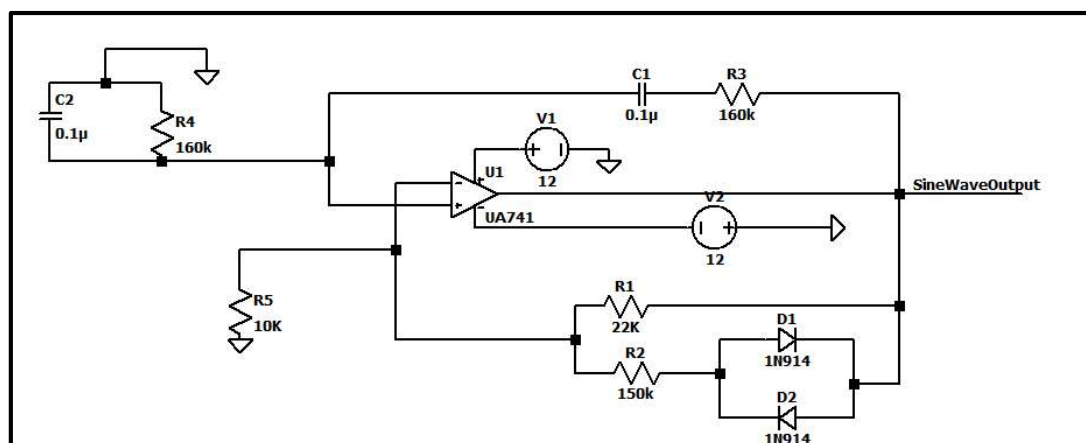


(ii) Square Wave:

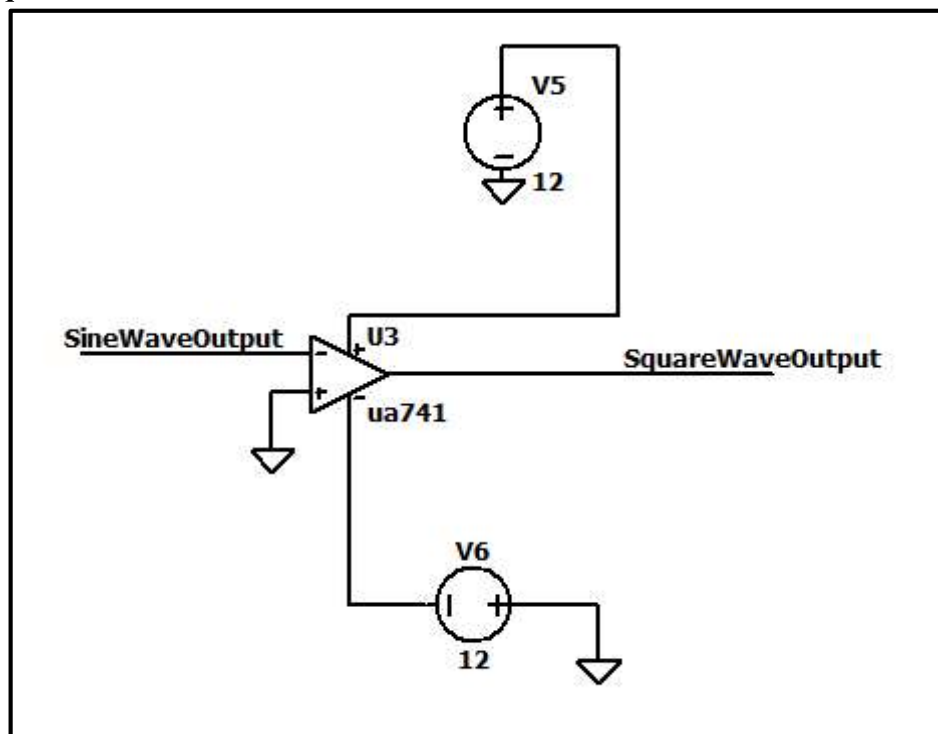


(iii) Triangle wave:

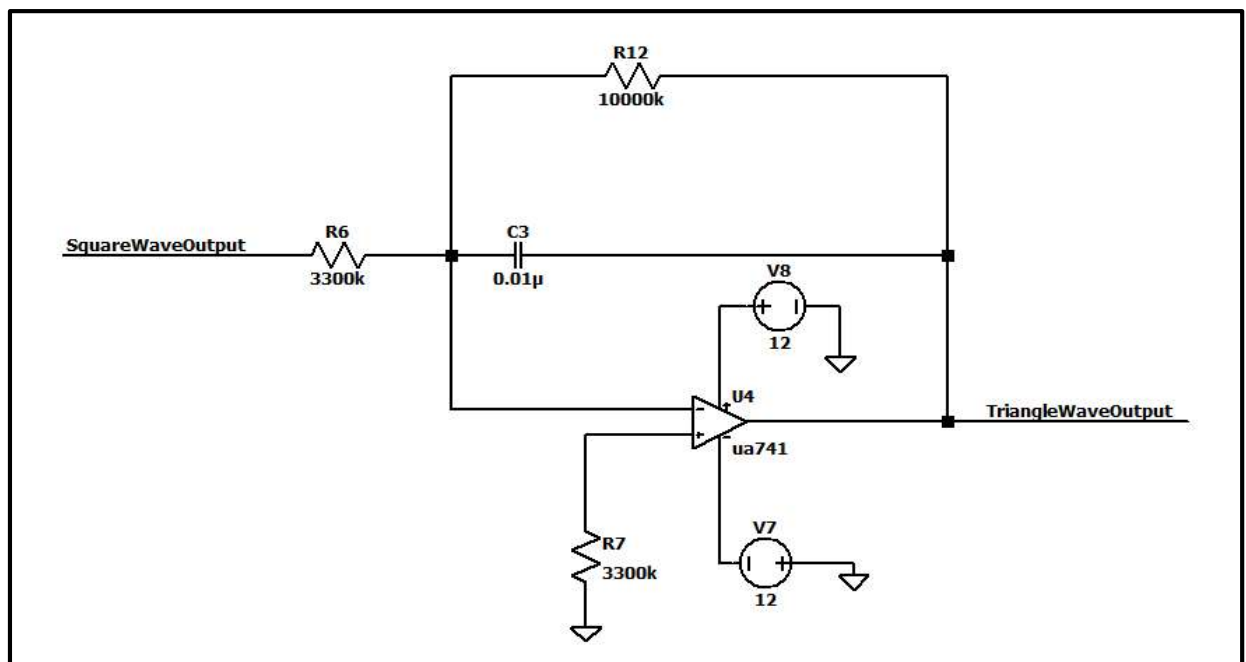


(iv) **Pulse Wave:**

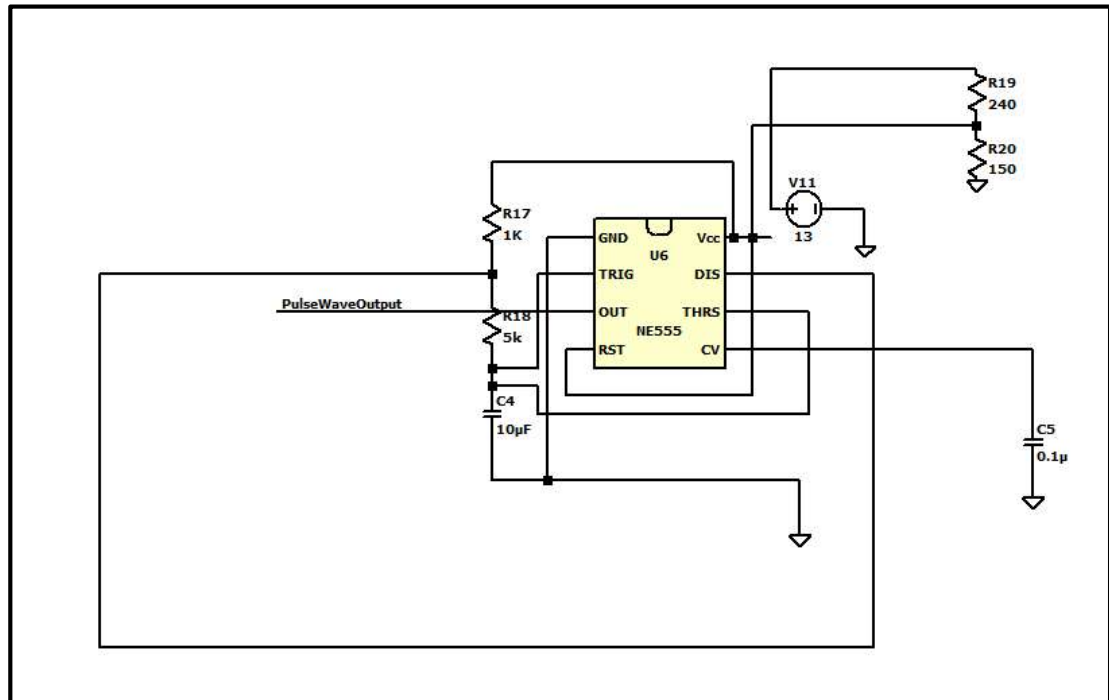


(v) **Gain Stage:**

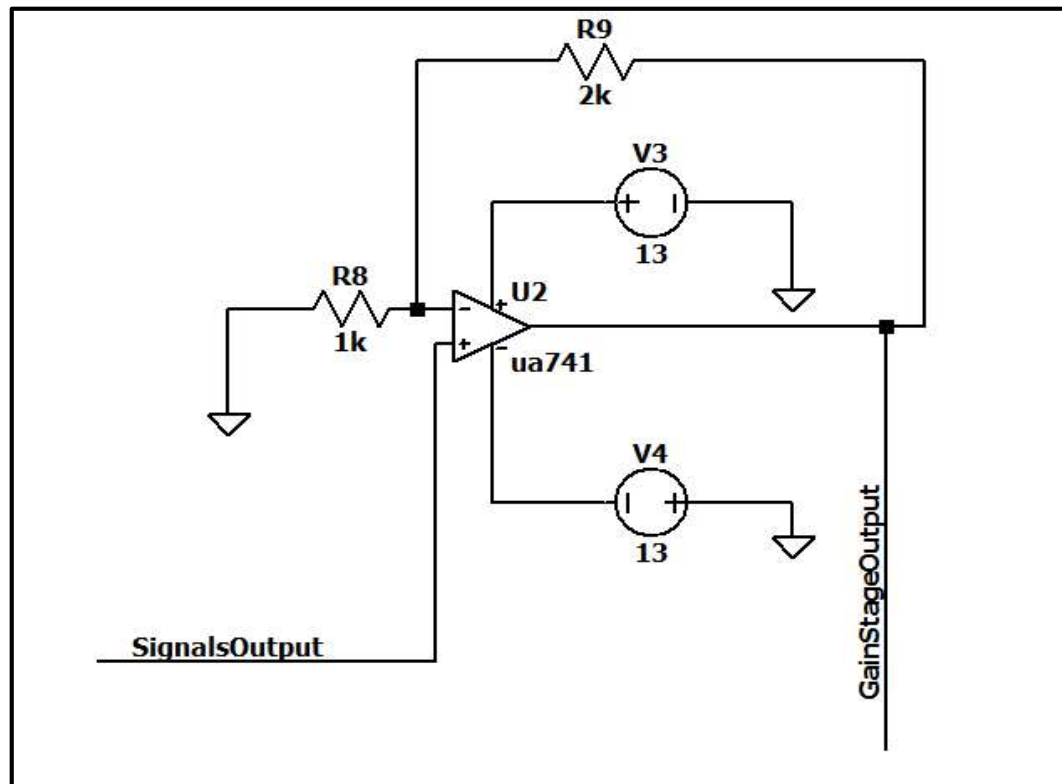

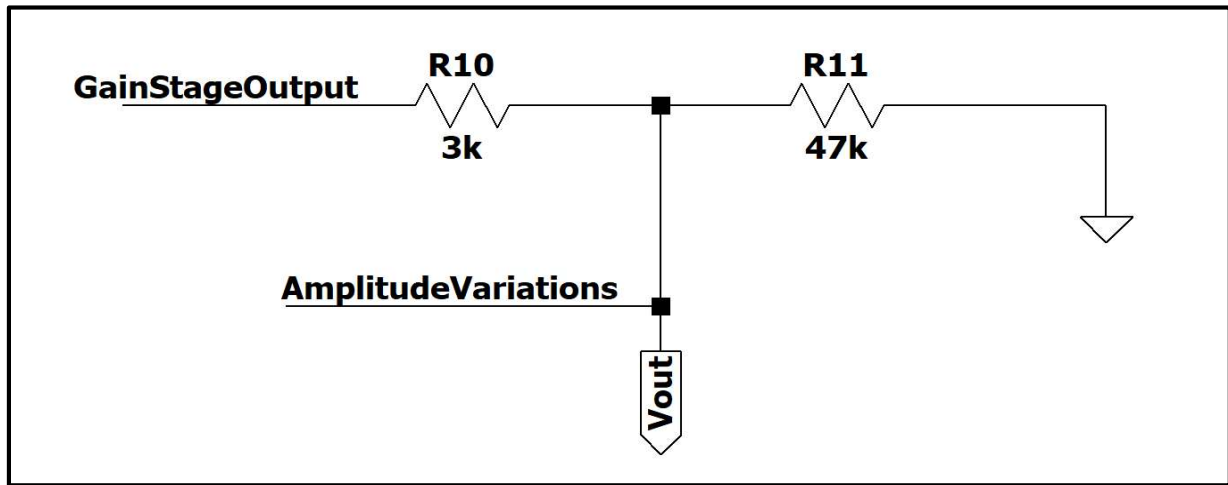(vi) Voltage Divider for amplitude variations:



(vii) Circuit Diagram:

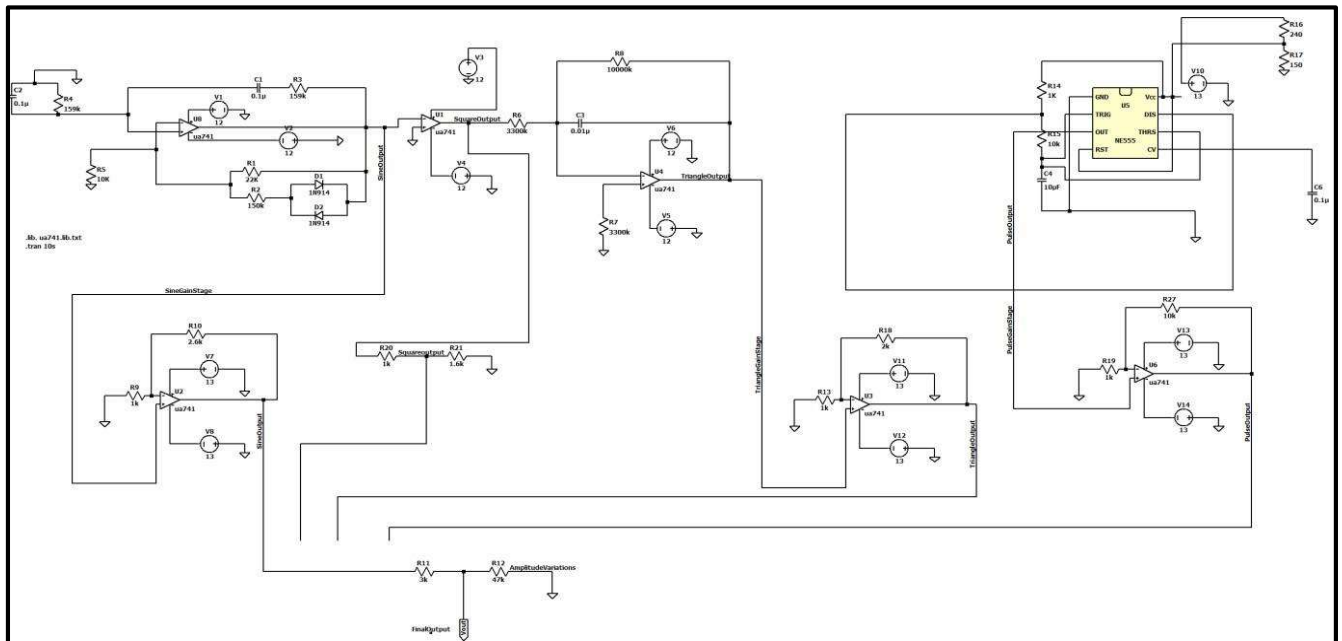

Simulation results for minimum frequency of 10Hz are below:

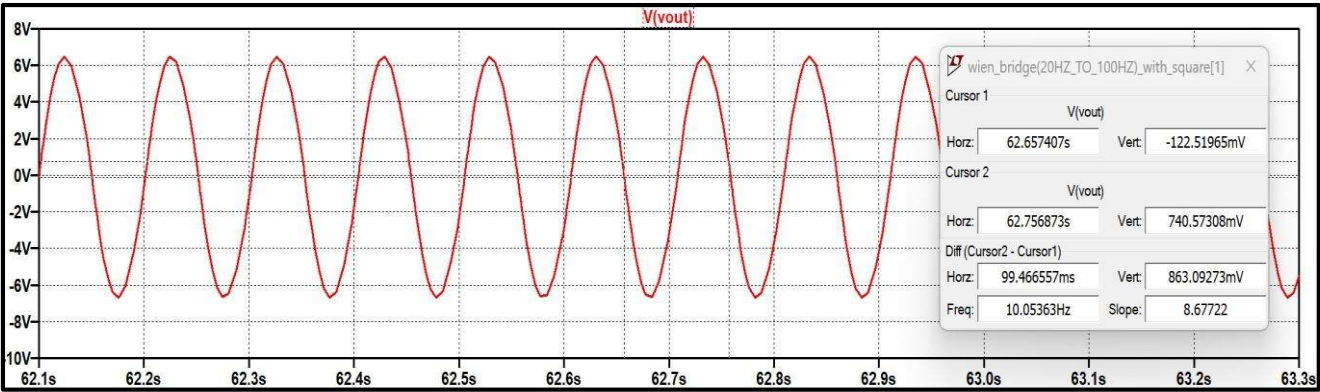


Fig. 1 Sine Wave Output

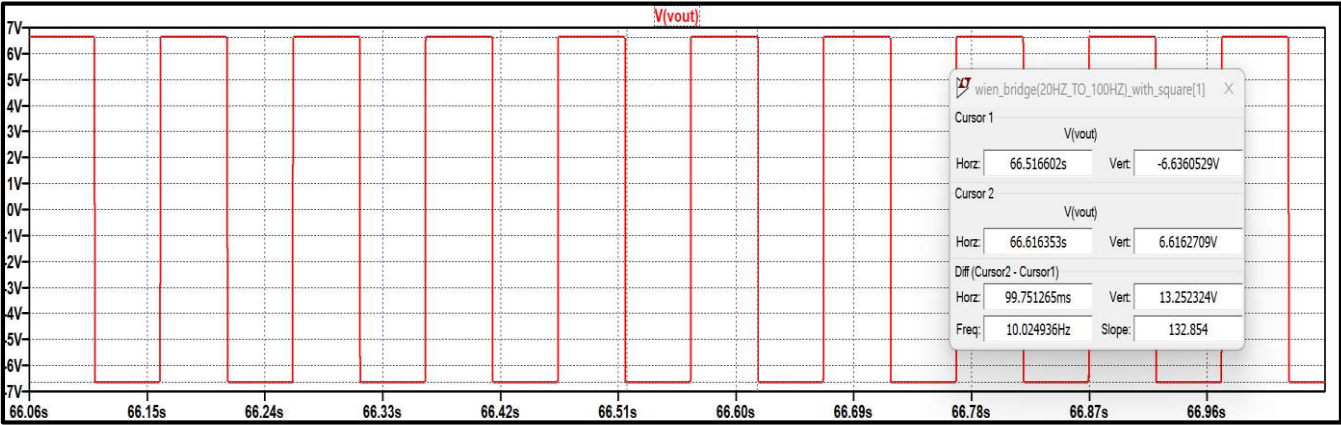


Fig. 2 Square Wave Output


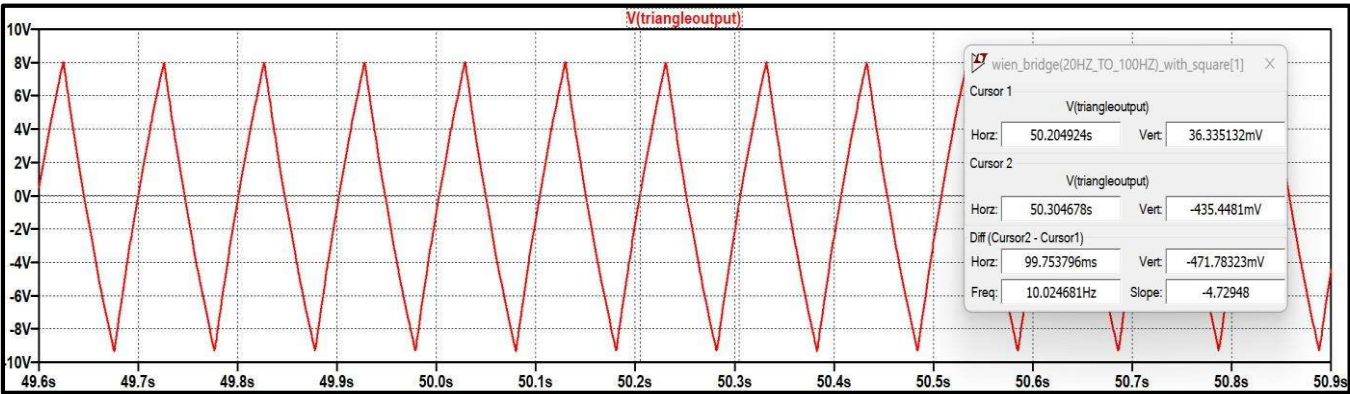



Fig. 3 Triangle Wave Output

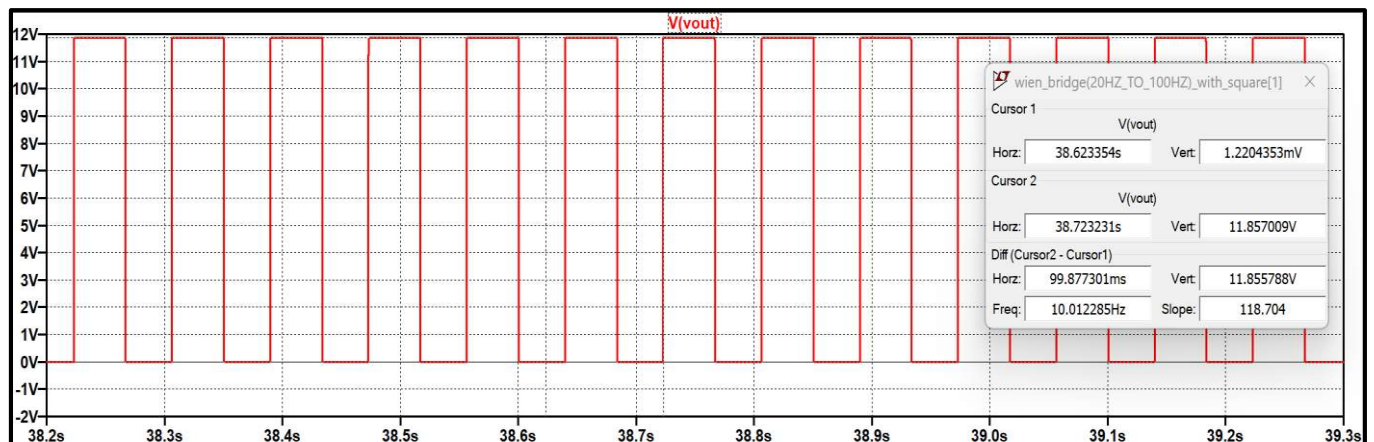



**Fig. 4 Pulse Wave Output**

## 7. Implementation / Prototyping results:

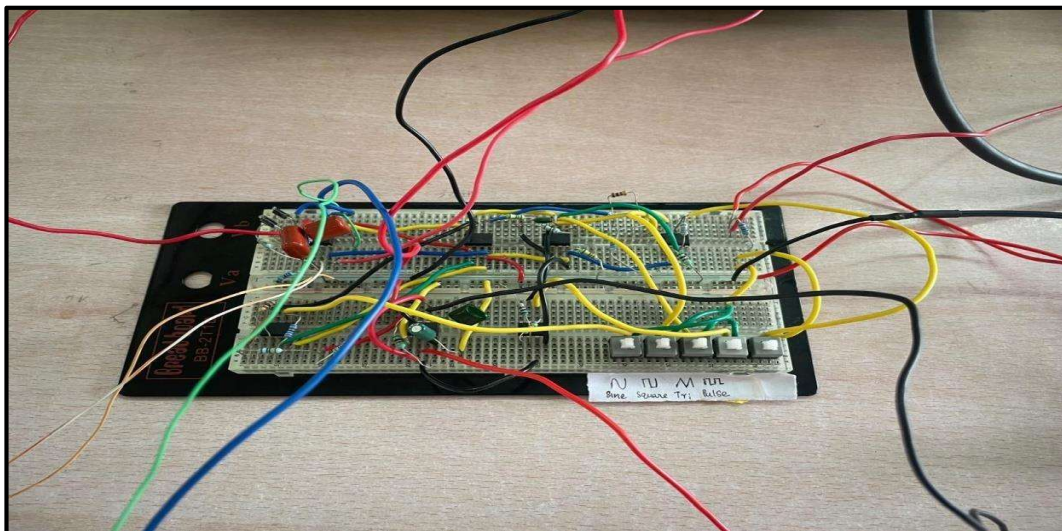

**Fig. 4 Hardware Circuit**

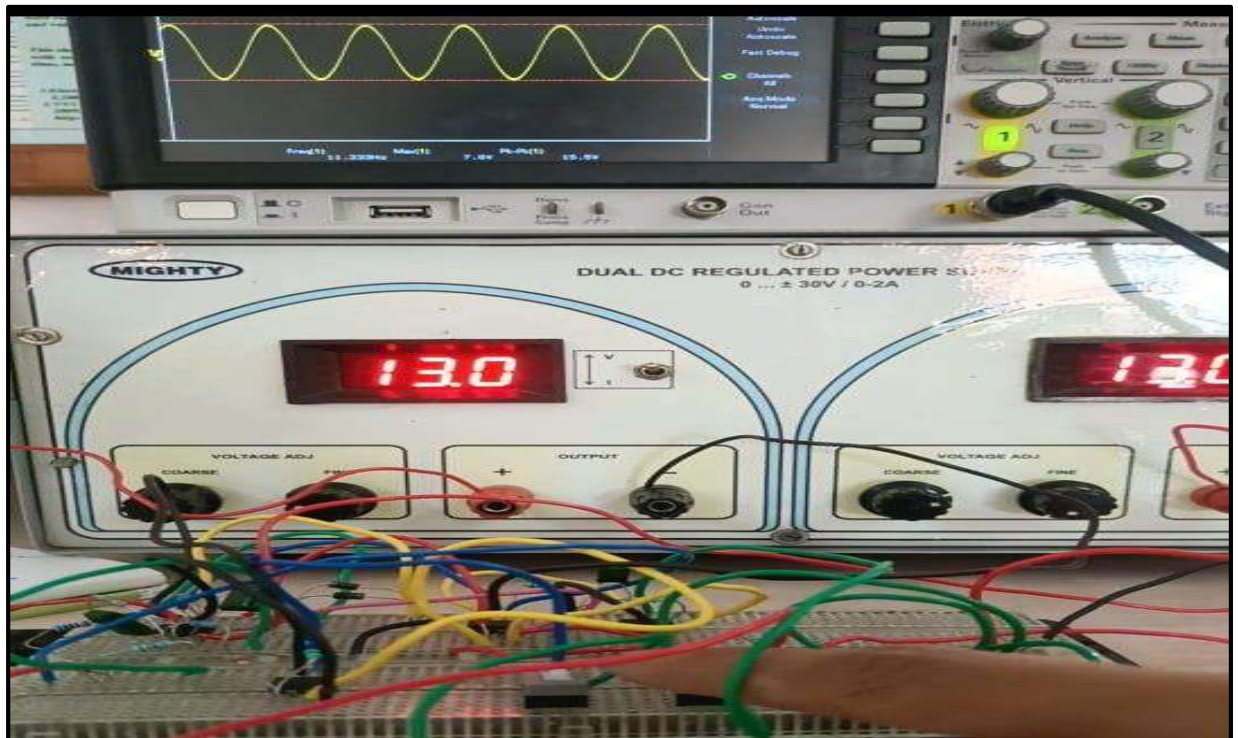


Fig. 5 Sine Wave Output


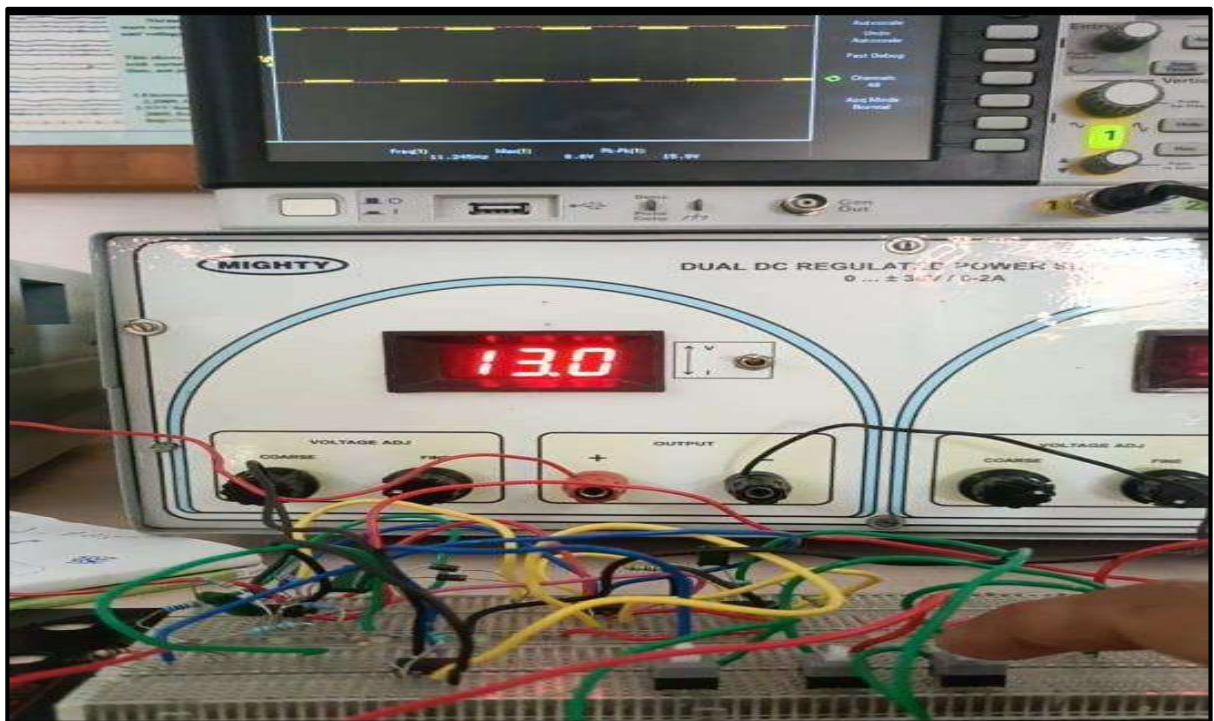


Fig. 6 Square Wave Output

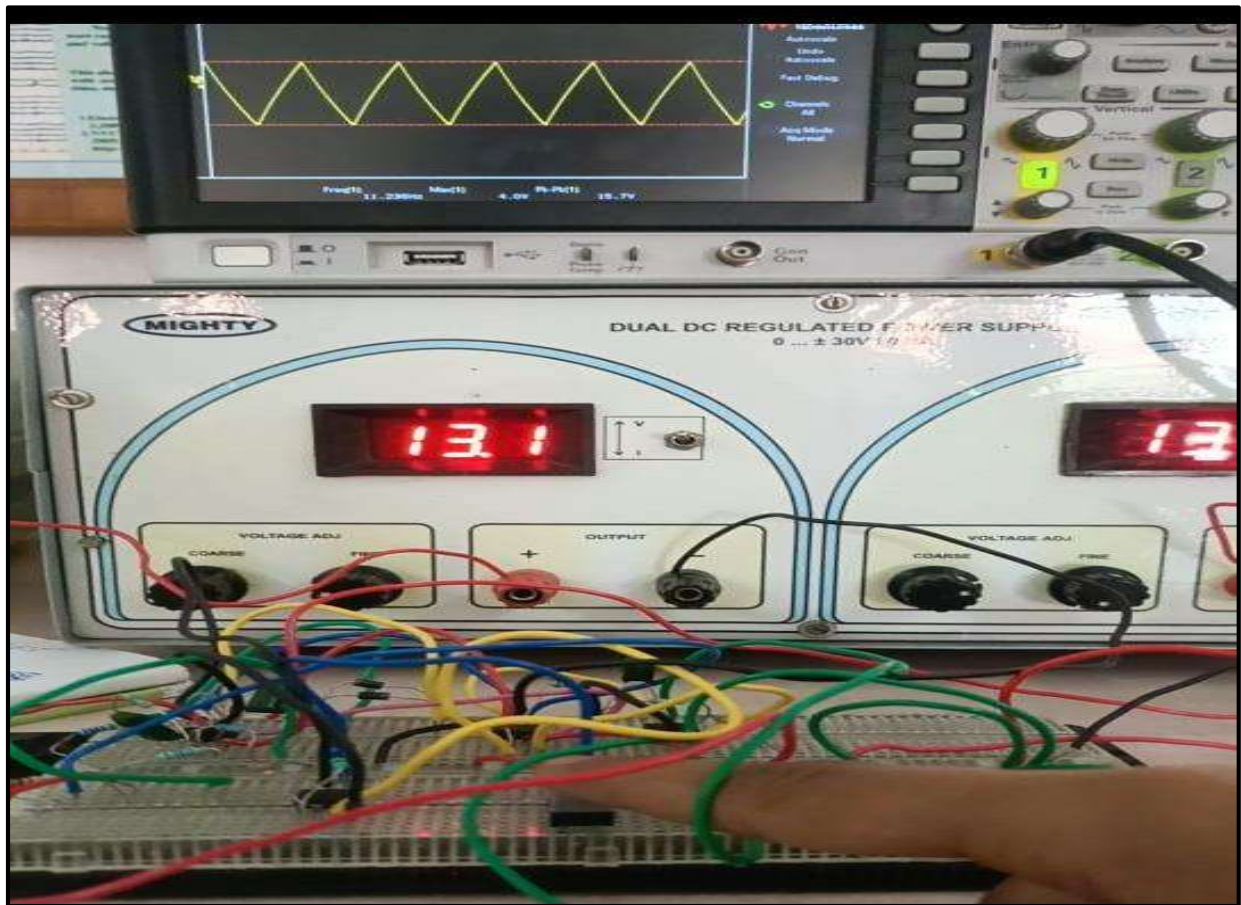



*Fig. 7 Triangle Wave Output*

8. **Discussion & Conclusions:** Our low frequency function generator yields the required wave upon the switch pressing labelled with corresponding wave and amplitude can be altered ( a minimum of 5V(p-p) is guaranteed by utilizing gain stages. The results could have been even more better if variable capacitor has been utilized as the potentiometer tuning in wien bridge stage for frequency variations is causing amplitude variations which could be resolved upon usage of variable capacitors which would provide a standard amplitude for a particular frequency.